

Comparator & Decoder

Monday, April 20, 2020 9:56 AM


1 0 0
1 0 1

Λ / √ 0
Λ / √ √


Λ Λ / √
Λ Λ / 0

A	B	f_2	f_3	f
0	0	0	1	0
0	1	1	0	0
1	0	0	0	1
1	1	0	1	0

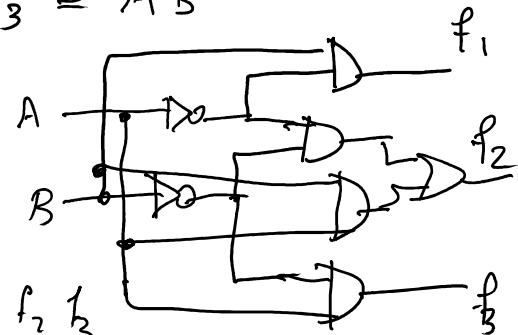$\textcircled{<} f_1 = A'B$
 $\textcircled{=} f_2 = A'B + AB = A \odot B = (A \oplus B)'$
 $\textcircled{>} f_3 = AB'$



A a₁ a₀
B b₁ b₀

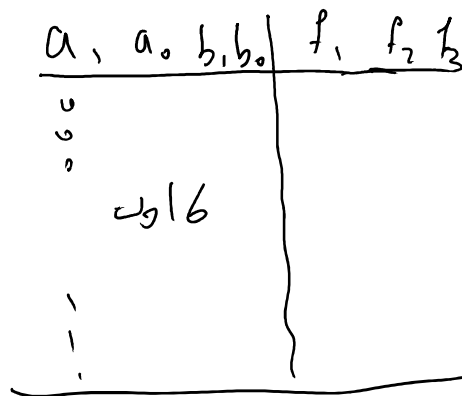


$x_1 = a_1 b_1 + a_1' b_1'$
 $x_0 = a_0 b_0 + a_0' b_0'$

$f_2 = (a_1 b_1 + a_1' b_1') (a_0 b_0 + a_0' b_0')$

f₁ a₁ a₀ b₁ b₀

$f_2 = x_1 x_0$
 A a₁ a₀ 1 0 f₁ = 1
 B b₁ b₀ 0 1 X

$f_1 = a_1' b_1 + (a_0' b_0) x_1$

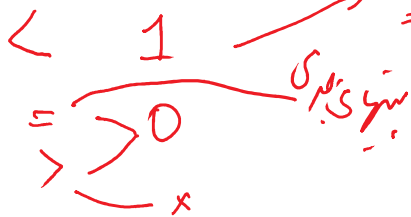

$f_1 = 0 + 0 \cdot 1 = 0$

$x_i = a_i b_i + a_i' b_i'$

— x

$$A = a_3 a_2 a_1 a_0$$

$$B = b_3 b_2 b_1 b_0$$



$$x_i = a_i b_i + a_i' b_i'$$

$i = 0, 1, 2, 3$

$$f_2 = x_0 x_1 x_2 x_3$$



$$f_1 = a_3' b_3 + x_3 \cdot (a_2' b_2) + x_3 x_2 (a_1' b_1) + x_3 x_2 x_1 (a_0' b_0)$$

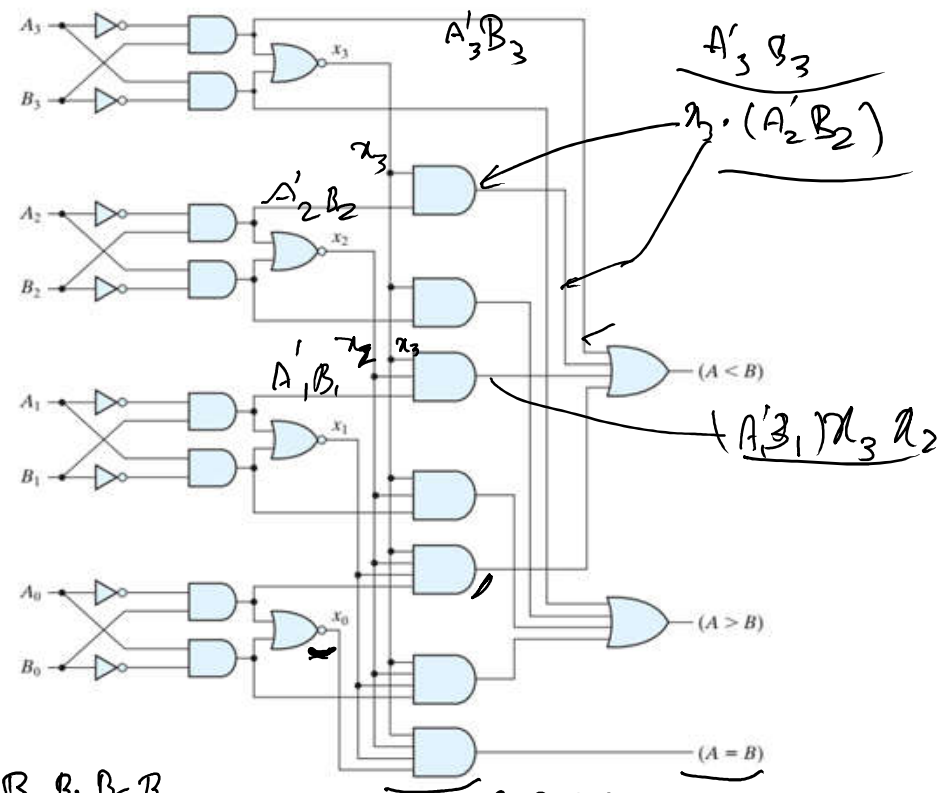
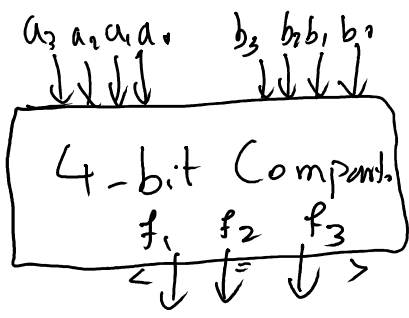
$$f_3 = a_3 b_3' + x_3 (a_2 b_2') + x_3 x_2 (a_1 b_1') + x_3 x_2 x_1 (a_0 b_0')$$



$$(A_0' B_0 + A_0 B_0)'$$

$$= A_0 B_0 + A_0' B_0'$$

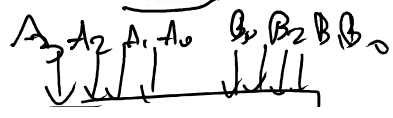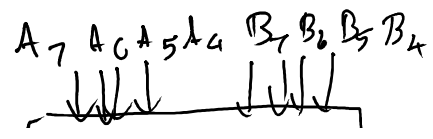

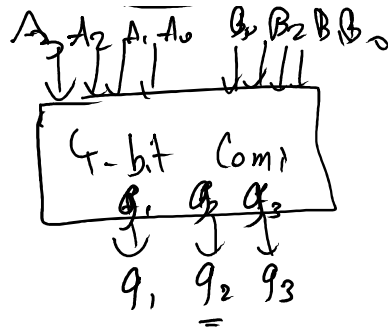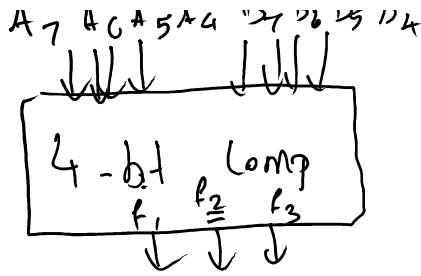

داتا کد
 اسی
 اسی

$$(A=B)F_2 = f_2 \cdot g_2$$


(Encoder)

دکودر (Decoder)

(Decoder/De multiplexer)


Decoder

n	→	2 ⁿ
2	→	4
3	→	8
4	→	16

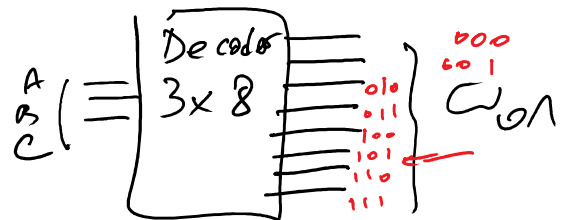

A	B	C
0	0	0

ن 10 |

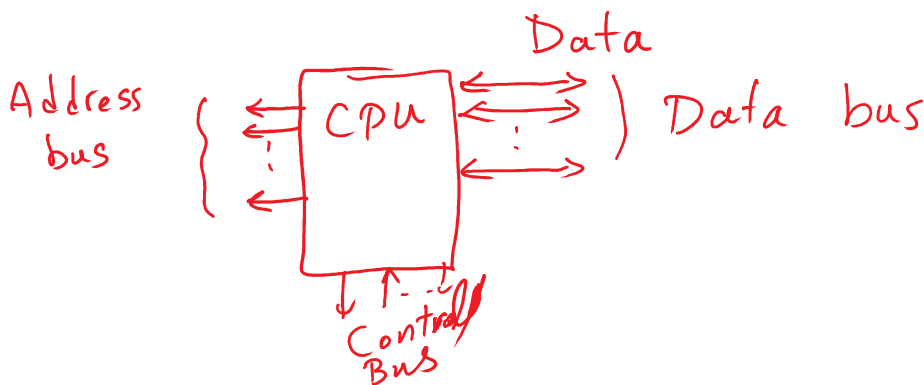

$$2^3 = 8$$


$$2^4 = 16$$

$$2^5 = 32$$

8

16

32

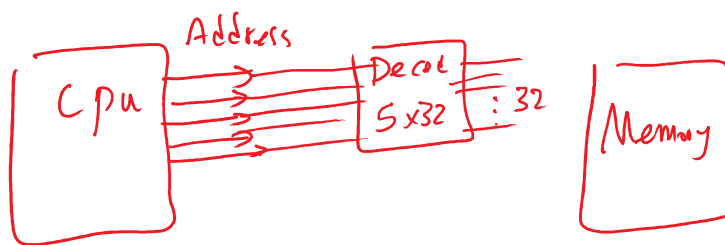

1 Mem

10 = 1k
 2²⁰ = 1M
 2³⁰ = 1G
 4 G byte





$2^{30} = 1G$
 $4G \text{ byte}$
 $2^2 \times 2^{30} = 2^{32} = 4G$




Decoder $n \times 2^n$

Decoder 3×8
 $m_0 = A'B'C'$
 $m_1 = A'B'C$


	A	B	C	m_0	m_1	D_2	D_3	D_4	D_5	D_6	D_7
m_0	0	0	0	1	0	0	0	0	0	0	0
m_1	0	0	1	0	1	0	0	0	0	0	0
m_2	0	1	0	0	0	1	0	0	0	0	0
m_3	0	1	1	0	0	0	1	0	0	0	0
m_4	1	0	0	0	0	0	0	1	0	0	0
m_5	1	0	1	0	0	0	0	0	1	0	0
m_6	1	1	0	0	0	0	0	0	0	1	0
m_7	1	1	1	0	0	0	0	0	0	0	1

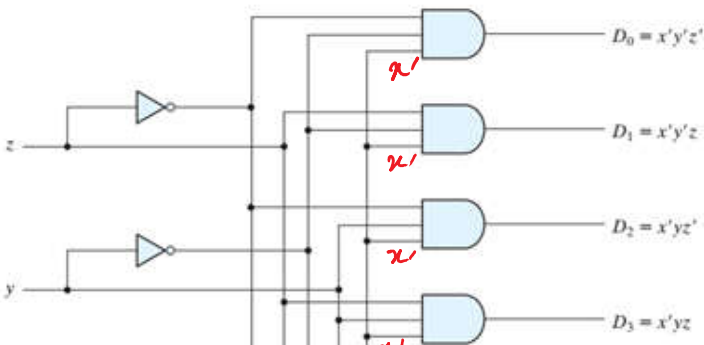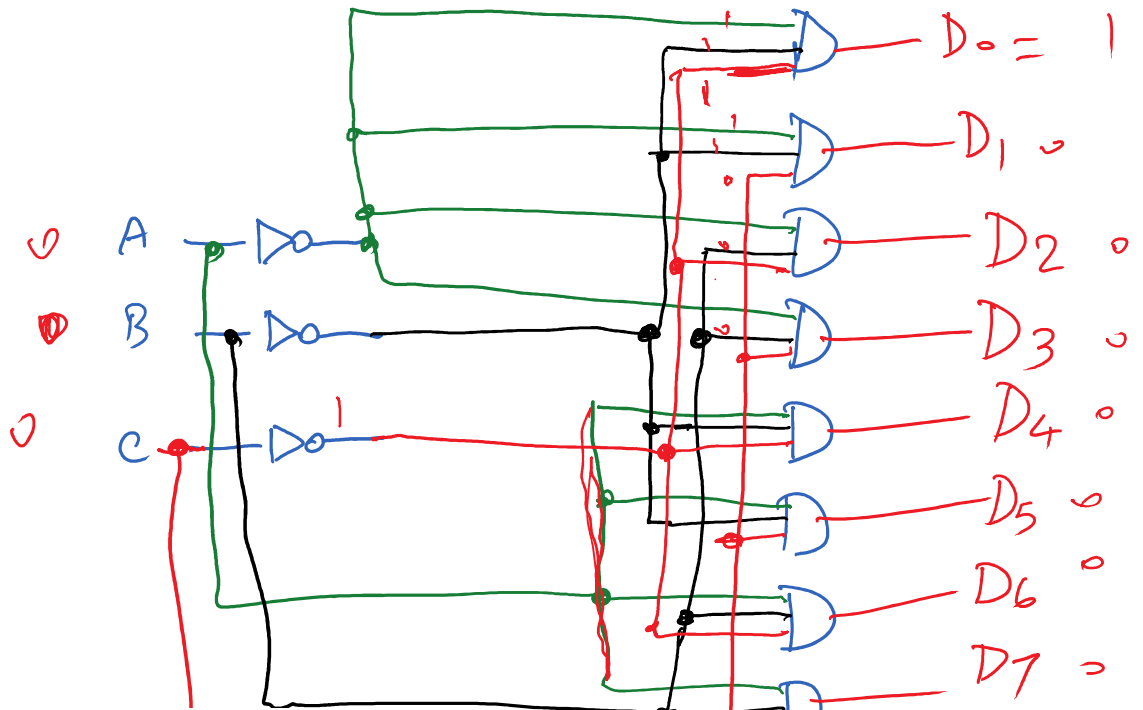

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0

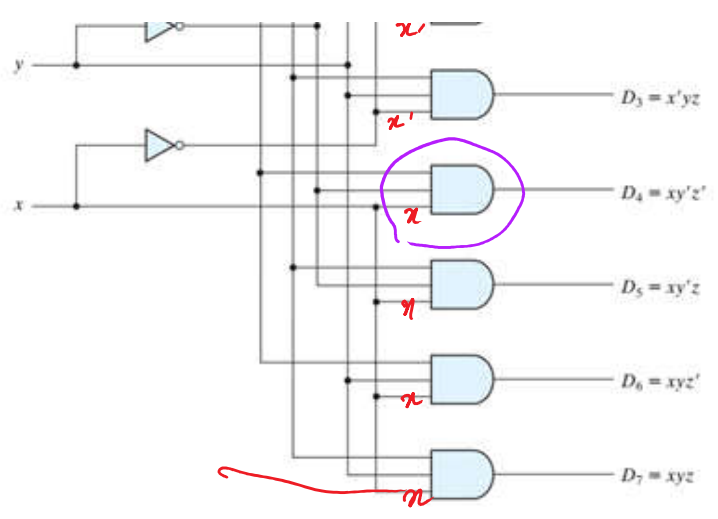


0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


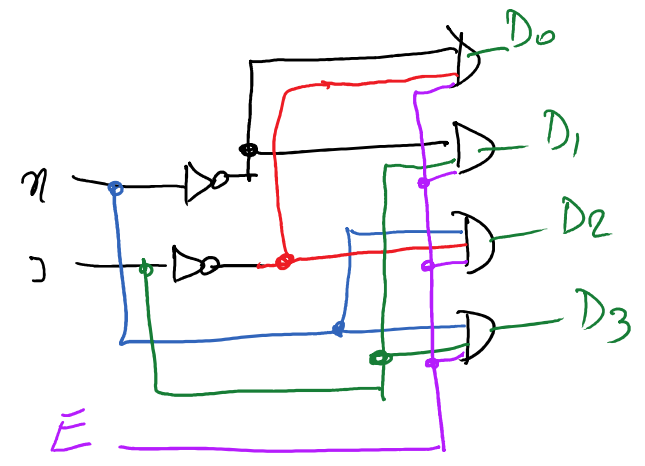


x	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


Enable
iindis iindis

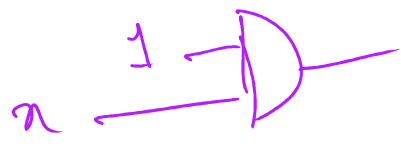

E 1 Decoder
E 0 0

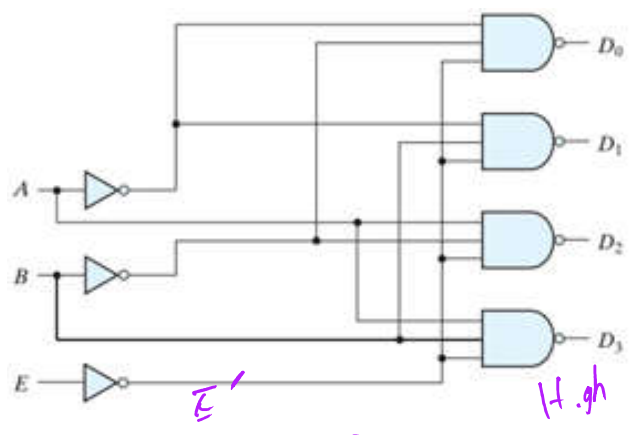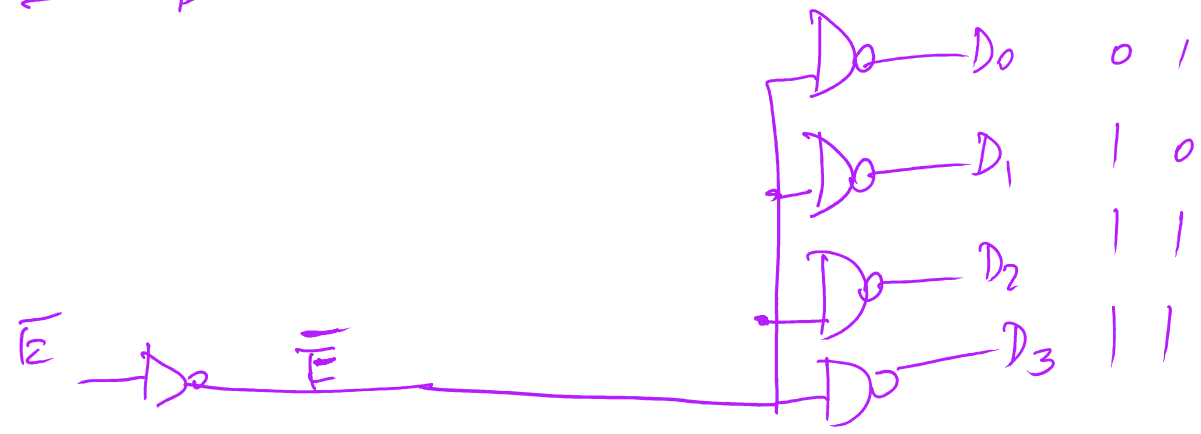

5 x 32

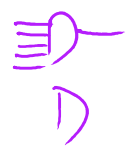

low Active

E	A	B	D ₀	D ₁	D ₂	D ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	1

NAND

E	A	B	D ₀	D ₁	D ₂	D ₃
0	X	X	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1

AND


32 :

Decoder 4x16



A
B
C
D

D
16
D

A	B	C	D
0	0	0	0
0	0	0	1
0	1	0	0
0	1	0	1
1	0	0	0
1	0	0	1
1	1	0	0
1	1	0	1

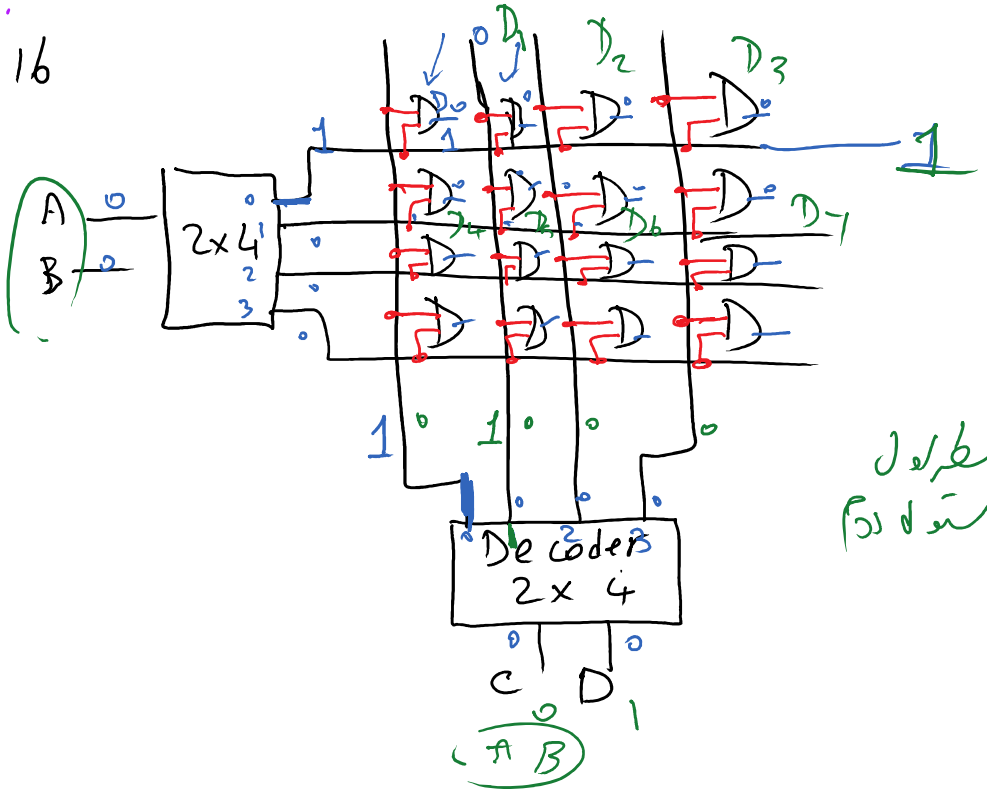

کامل شده است

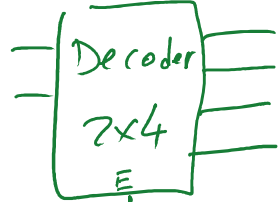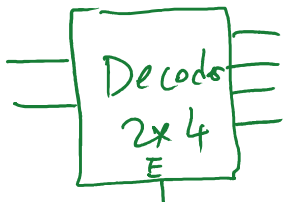


Decoder 2x4

x	y	z
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

D₀
D₁
D₂
D₃
D₄

Decoder 3x8

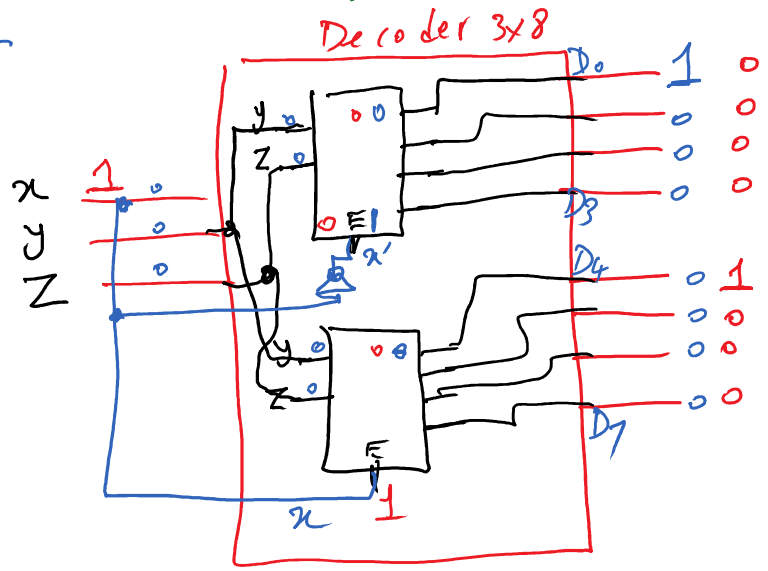

3x8 3x8

4x16

با دو کدی

