

$$F = \underbrace{A'B'C'}_{m_0} + \underbrace{B'CD'}_{m_6} + \underbrace{A'BCD'}_{m_2} + \underbrace{AB'C'}_{m_4}$$

$$A'B'C' = A'B'C'(D'+D)$$

$$= A'B'C'D' + A'B'C'D$$


$m_0 + m_1$

$$B'CD' = B'CD'(A'+A)$$

$$= A'B'CD' + AB'CD'$$


$m_2 + m_{10}$
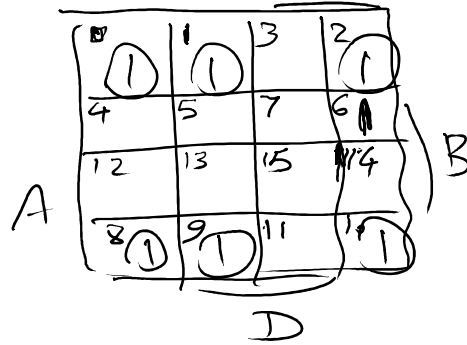
$$AB'C' = AB'C'(D'+D) = AB'C'D' + AB'C'D$$





$$F = \sum (0, 1, 2, 10, 8, 9, 6)$$

$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$

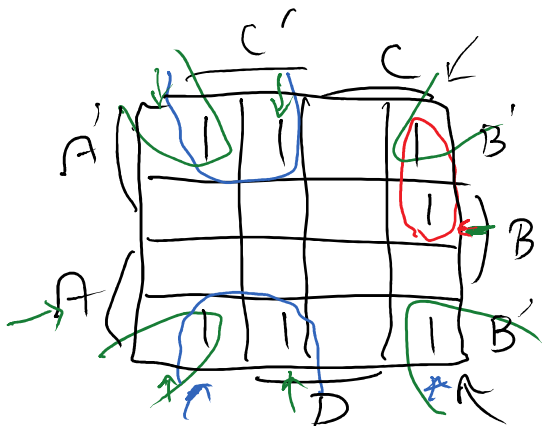
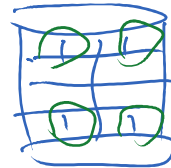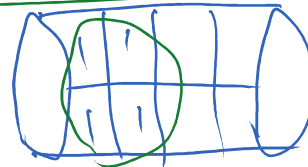
$$F = \underbrace{B'C'} + \underbrace{B'D'} + \underbrace{A'CD'}$$





Don't care \bar{c} \bar{c}

Simplify the Boolean function


$$F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$$


which has the don't-care conditions

$$d(w, x, y, z) = \sum(0, 2, 5)$$

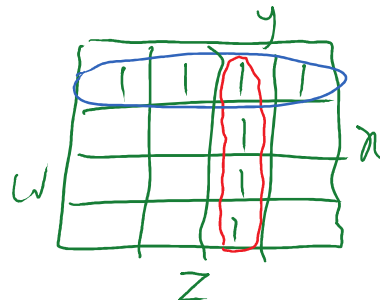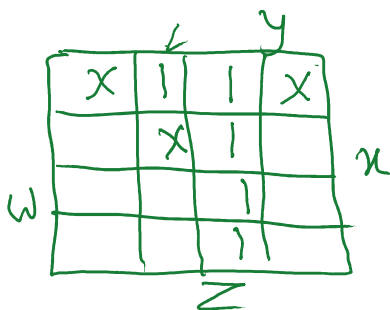

$$F = yz + w'x'$$

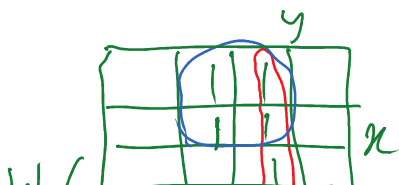



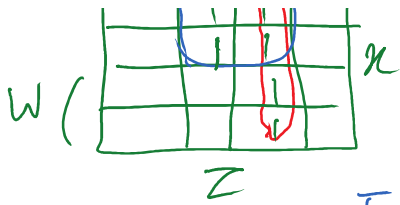


$$F = yz + wz$$

$$F = yz + w'z$$



$$F = A'B'C' + B'CD' + A'BCD' + AB'C'$$
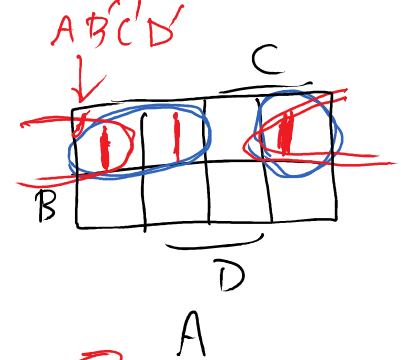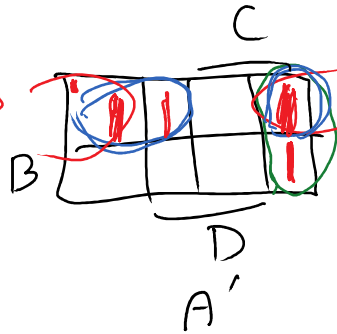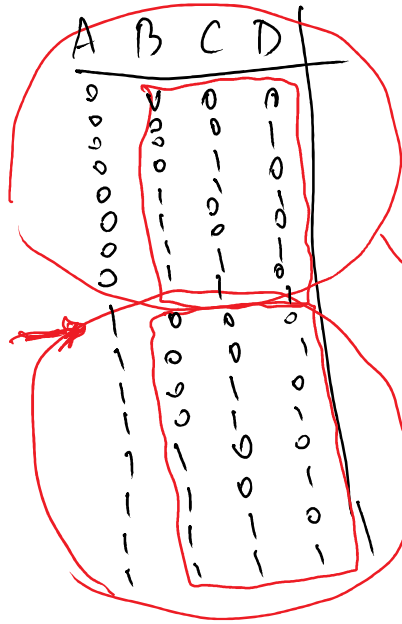
$$F(A, B, C, D) = \sum (0, 1, 2, 6, 8, 9, 10)$$



$$A'CD' + B'C' + B'D'$$
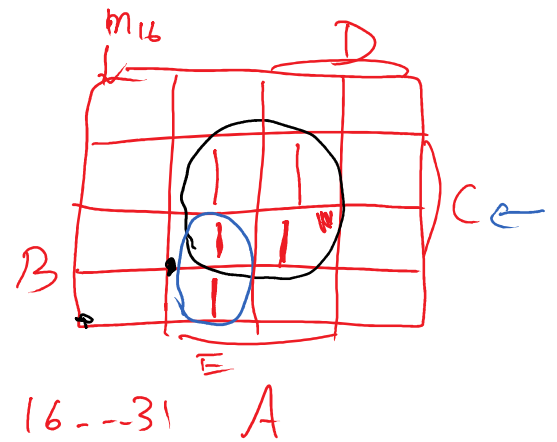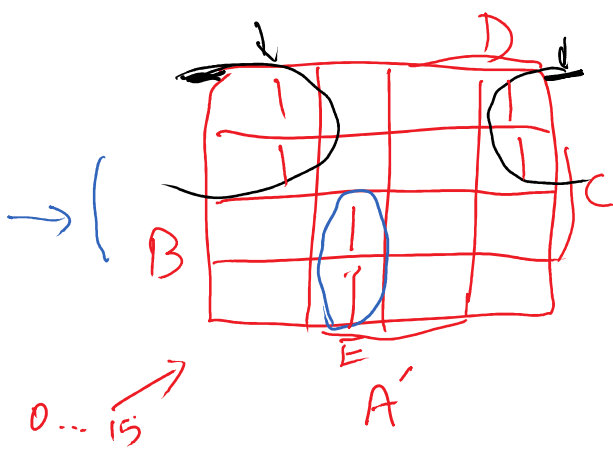
$$F(A, B, C, D, E) = \sum (0, 2, 4, 6, 9, 13, 21, 23, 25, 29, 31)$$



$$F = BD'E + A'B'E + ACE$$

	A	B	C	F
m_0	0	0	0	0
$\rightarrow m_1$	0	0	1	1
$\rightarrow m_2$	0	1	0	1
m_3	0	1	1	0
$\rightarrow m_4$	1	0	0	1

$$F = A \oplus B \oplus C$$


$\sum (1, 2, 4, 7)$ odd

$$F = (A \oplus B \oplus C)'$$

$$\begin{array}{l} m_3 \ 0 \ 1 \ 1 \ | \ 0 \\ \rightarrow m_4 \ 1 \ 0 \ 0 \ | \ 1 \\ m_5 \ 1 \ 0 \ 1 \ | \ 0 \\ m_6 \ 1 \ 1 \ 0 \ | \ 0 \\ m_7 \ 1 \ 1 \ 1 \ | \ 1 \end{array}$$

$$F = (A \oplus B \oplus C)^{\uparrow} \text{ even } n$$

$$\Sigma(0, 3, 5, 6)$$

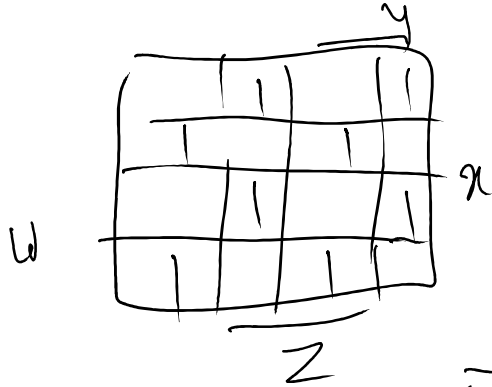


$$1101 = 13$$

$$1011 = 11$$

$$1110 = 14$$


$$F = w \oplus x \oplus y \oplus z$$
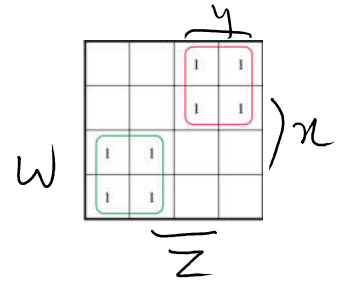
$$\begin{aligned} \bar{F} &= wy' + w'y \\ &= w \oplus y \end{aligned}$$



$$\begin{aligned} F &= wy'z' + wyz \\ &\quad + w'y'z + w'yz' \\ &= w(y'z' + yz) + \\ &\quad w'(y'z + yz') \end{aligned}$$
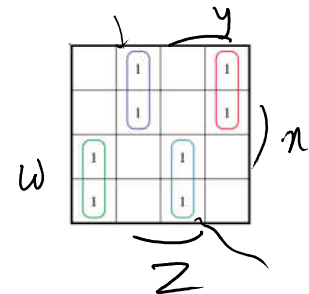
$$= wA' + w'A = w \oplus A = w \oplus y \oplus z$$



$$A = y'z + yz'$$

$$= y \oplus z$$